

**CSE 305: Computer Architecture**  
Class Test 3, July 2015


**Time: 20 minutes**

**Full Marks: 20**

Name:	Student No.:
-------	--------------

 1. The basic instruction fetch unit of MIPS computer system is given below. Please add the necessary elements to it so that it can incorporate-

- general sequential execution 2
- “beq” instruction execution 2
- “j” instruction execution 3



2. A simple MIPS datapath and its respective control signals are illustrated below. Please design the control bits corresponding to the instruction “sw rt, 0(rs)”  $6 \times \frac{1}{2} = 3$  for this datapath.

Control Signal	0	1	<b>SW</b>
RegDst	Write register address = rt	Write register address = rd	
RegWrite	-	Write register	
ALUSrc	ALU Second Operand = Read data 2	ALU Second Operand = lower 16-bit of instruction	
MemRead	-	Read data from memory	
MemWrite	-	Write data into memory	
MementoReg	Register Write Data from ALU	Register Write Data from data memory	

