


CSE 305: Computer Architecture


Tanvir Ahmed Khan
takhandipu@gmail.com


Department of Computer Science and Engineering
Bangladesh University of Engineering and Technology.


November 8, 2015

Recap

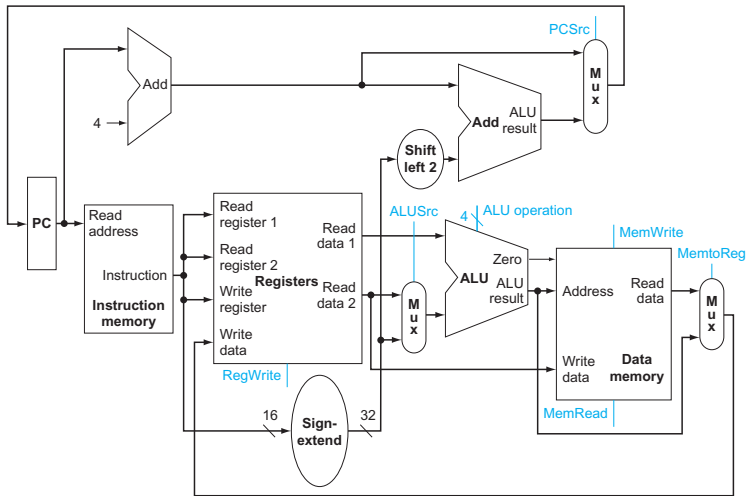

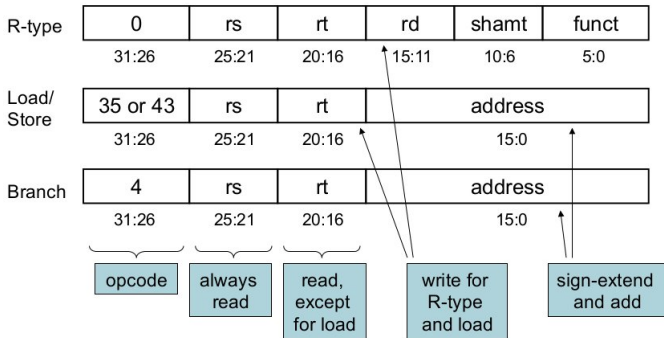

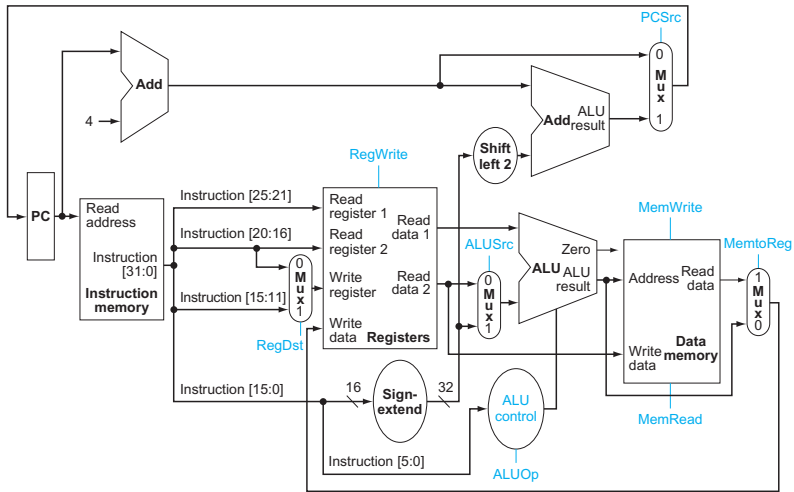

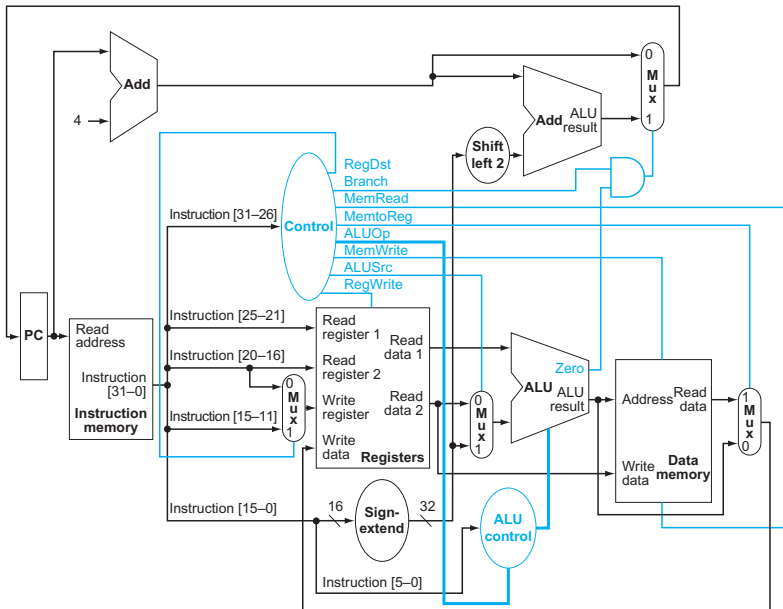


Today's Topic


Control Unit

Control Signal Summary

Control Signal	0	1
RegDst	Write register address = rt	Write register address = rd
RegWrite	-	Write register
AluSrc	ALU Second Operand = Read data 2	ALU Second Operand = lower 16-bit of instruction
PCSrc	PC=PC+4	PC=branch target
MemRead	-	Read data from memory
MemWrite	-	Write data into memory
MemtoReg	Register Write Data from ALU	Register Write Data from data memory

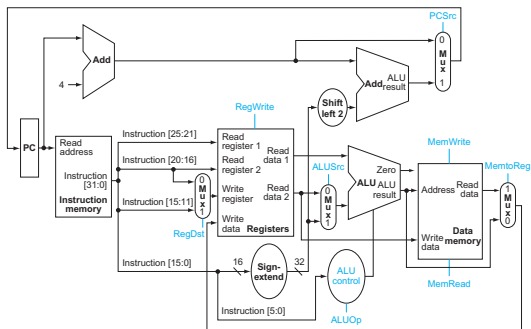


Control Signal	0	1
RegDst	Write register address = rt	Write register address = rd
RegWrite	-	Write register
AluSrc	ALU Second Operand = Read data 2	ALU Second Operand = lower 16-bit of instruction
PCSrc	PC=PC+4	PC=branch target
MemRead	-	Read data from memory
MemWrite	-	Write data into memory
MemtoReg	Register Write Data from ALU	Register Write Data from data memory

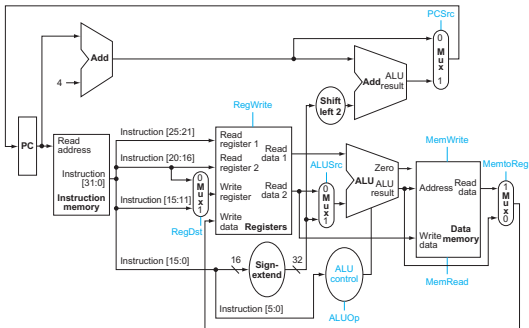

lw rt, 0(rs)

lw	RegDst	RegWrite	ALUSrc	PCSrc	MemRead	MemWrite	MemtoReg


Control Signal	0	1
RegDst	Write register address = rt	Write register address = rd
RegWrite	-	Write register
AluSrc	ALU Second Operand = Read data 2	ALU Second Operand = lower 16-bit of instruction
PCSrc	PC=PC+4	PC=branch target
MemRead	-	Read data from memory
MemWrite	-	Write data into memory
MemtoReg	Register Write Data from ALU	Register Write Data from data memory

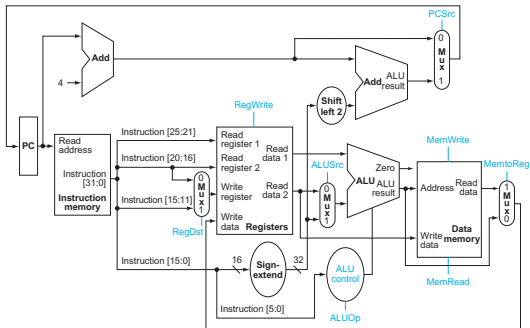

lw rt, 0(rs)

lw	RegDst	RegWrite	ALUSrc	PCSrc	MemRead	MemWrite	MemtoReg
	0						


Control Signal	0	1
RegDst	Write register address = rt	Write register address = rd
RegWrite	-	Write register
AluSrc	ALU Second Operand = Read data 2	ALU Second Operand = lower 16-bit of instruction
PCSrc	PC=PC+4	PC=branch target
MemRead	-	Read data from memory
MemWrite	-	Write data into memory
MemtoReg	Register Write Data from ALU	Register Write Data from data memory

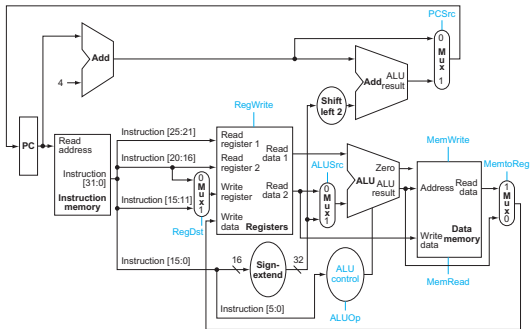

lw rt, 0(rs)

	RegDst	RegWrite	ALUSrc	PCSrc	MemRead	MemWrite	MemtoReg
lw	0	1					


Control Signal	0	1
RegDst	Write register address = rt	Write register address = rd
RegWrite	-	Write register
AluSrc	ALU Second Operand = Read data 2	ALU Second Operand = lower 16-bit of instruction
PCSrc	PC=PC+4	PC=branch target
MemRead	-	Read data from memory
MemWrite	-	Write data into memory
MemtoReg	Register Write Data from ALU	Register Write Data from data memory

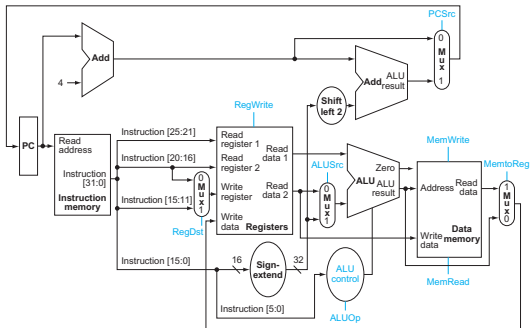

lw rt, 0(rs)

	RegDst	RegWrite	ALUSrc	PCSrc	MemRead	MemWrite	MemtoReg
lw	0	1	1				


Control Signal	0	1
RegDst	Write register address = rt	Write register address = rd
RegWrite	-	Write register
AluSrc	ALU Second Operand = Read data 2	ALU Second Operand = lower 16-bit of instruction
PCSrc	PC=PC+4	PC=branch target
MemRead	-	Read data from memory
MemWrite	-	Write data into memory
MemtoReg	Register Write Data from ALU	Register Write Data from data memory

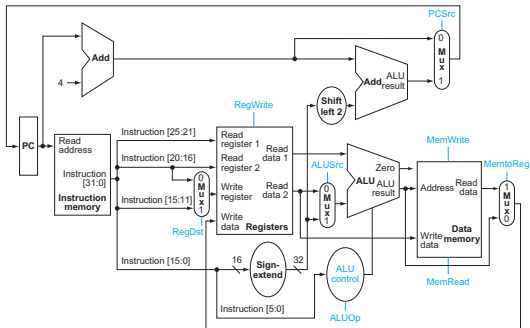

lw rt, 0(rs)

lw	RegDst	RegWrite	ALUSrc	PCSrc	MemRead	MemWrite	MemtoReg
	0	1	1	0			


Control Signal	0	1
RegDst	Write register address = rt	Write register address = rd
RegWrite	-	Write register
AluSrc	ALU Second Operand = Read data 2	ALU Second Operand = lower 16-bit of instruction
PCSrc	PC=PC+4	PC=branch target
MemRead	-	Read data from memory
MemWrite	-	Write data into memory
MemtoReg	Register Write Data from ALU	Register Write Data from data memory

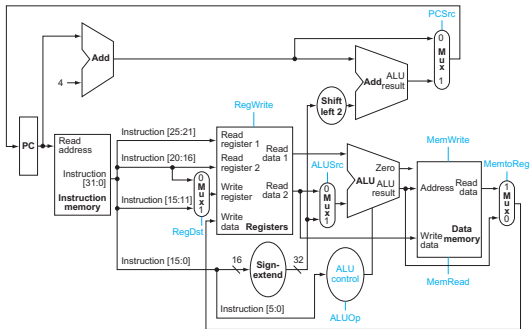

lw rt, 0(rs)

lw	RegDst	RegWrite	ALUSrc	PCSrc	MemRead	MemWrite	MemtoReg
	0	1	1	0	1		


Control Signal	0	1
RegDst	Write register address = rt	Write register address = rd
RegWrite	-	Write register
AluSrc	ALU Second Operand = Read data 2	ALU Second Operand = lower 16-bit of instruction
PCSrc	PC=PC+4	PC=branch target
MemRead	-	Read data from memory
MemWrite	-	Write data into memory
MemtoReg	Register Write Data from ALU	Register Write Data from data memory

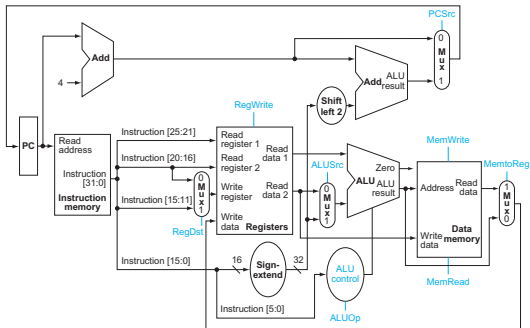

`lw rt, 0(rs)`

lw	RegDst	RegWrite	ALUSrc	PCSrc	MemRead	MemWrite	MemtoReg
	0	1	1	0	1	0	


Control Signal	0	1
RegDst	Write register address = rt	Write register address = rd
RegWrite	-	Write register
AluSrc	ALU Second Operand = Read data 2	ALU Second Operand = lower 16-bit of instruction
PCSrc	PC=PC+4	PC=branch target
MemRead	-	Read data from memory
MemWrite	-	Write data into memory
MemtoReg	Register Write Data from ALU	Register Write Data from data memory

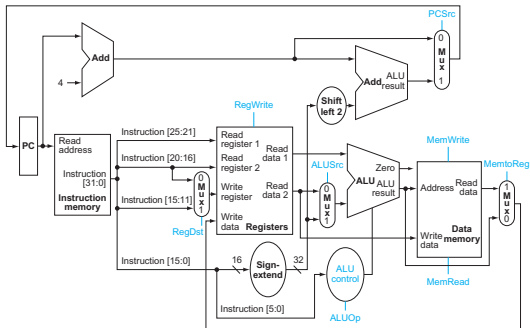

lw rt, 0(rs)

	RegDst	RegWrite	ALUSrc	PCSrc	MemRead	MemWrite	MemtoReg
lw	0	1	1	0	1	0	1


Control Signal	0	1
RegDst	Write register address = rt	Write register address = rd
RegWrite	-	Write register
AluSrc	ALU Second Operand = Read data 2	ALU Second Operand = lower 16-bit of instruction
PCSrc	PC=PC+4	PC=branch target
MemRead	-	Read data from memory
MemWrite	-	Write data into memory
MemtoReg	Register Write Data from ALU	Register Write Data from data memory

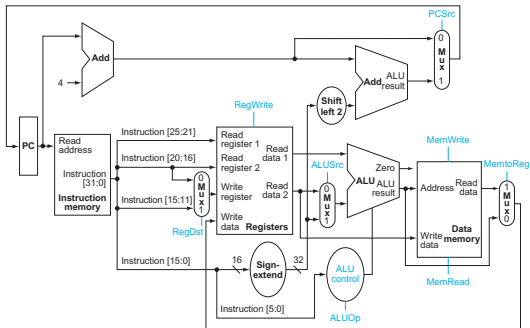

sw rt, 0(rs)

sw	RegDst	RegWrite	ALUSrc	PCSrc	MemRead	MemWrite	MemtoReg


Control Signal	0	1
RegDst	Write register address = rt	Write register address = rd
RegWrite	-	Write register
AluSrc	ALU Second Operand = Read data 2	ALU Second Operand = lower 16-bit of instruction
PCSrc	PC=PC+4	PC=branch target
MemRead	-	Read data from memory
MemWrite	-	Write data into memory
MemtoReg	Register Write Data from ALU	Register Write Data from data memory

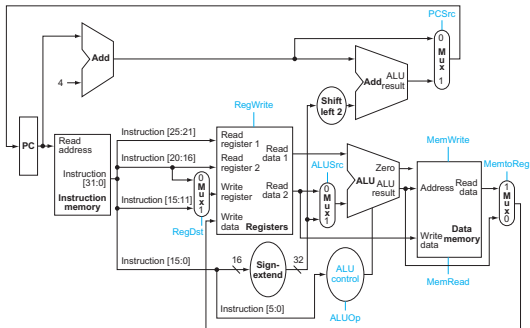

sw rt, 0(rs)

sw	RegDst	RegWrite	ALUSrc	PCSrc	MemRead	MemWrite	MemtoReg
	x						


Control Signal	0	1
RegDst	Write register address = rt	Write register address = rd
RegWrite	-	Write register
AluSrc	ALU Second Operand = Read data 2	ALU Second Operand = lower 16-bit of instruction
PCSrc	PC=PC+4	PC=branch target
MemRead	-	Read data from memory
MemWrite	-	Write data into memory
MemtoReg	Register Write Data from ALU	Register Write Data from data memory

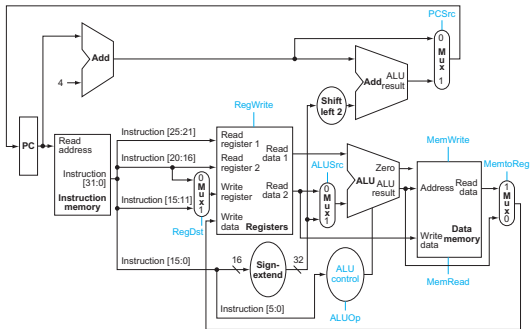

sw rt, 0(rs)

	RegDst	RegWrite	ALUSrc	PCSrc	MemRead	MemWrite	MemtoReg
sw	x	0					


Control Signal	0	1
RegDst	Write register address = rt	Write register address = rd
RegWrite	-	Write register
AluSrc	ALU Second Operand = Read data 2	ALU Second Operand = lower 16-bit of instruction
PCSrc	PC=PC+4	PC=branch target
MemRead	-	Read data from memory
MemWrite	-	Write data into memory
MemtoReg	Register Write Data from ALU	Register Write Data from data memory

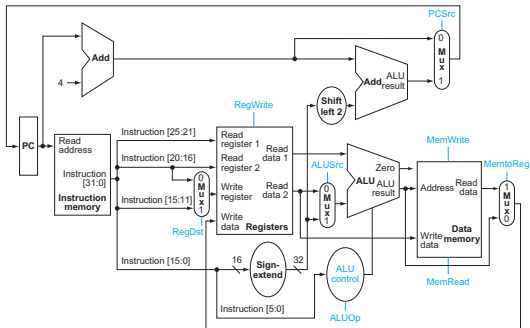

sw rt, 0(rs)

	RegDst	RegWrite	ALUSrc	PCSrc	MemRead	MemWrite	MemtoReg
sw	x	0	1				


Control Signal	0	1
RegDst	Write register address = rt	Write register address = rd
RegWrite	-	Write register
AluSrc	ALU Second Operand = Read data 2	ALU Second Operand = lower 16-bit of instruction
PCSrc	PC=PC+4	PC=branch target
MemRead	-	Read data from memory
MemWrite	-	Write data into memory
MemtoReg	Register Write Data from ALU	Register Write Data from data memory

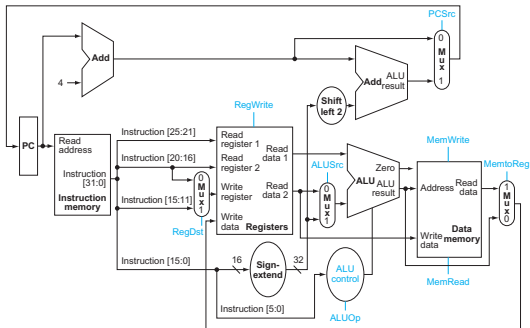

sw rt, 0(rs)

sw	RegDst	RegWrite	ALUSrc	PCSrc	MemRead	MemWrite	MemtoReg
	x	0	1	0			


Control Signal	0	1
RegDst	Write register address = rt	Write register address = rd
RegWrite	-	Write register
AluSrc	ALU Second Operand = Read data 2	ALU Second Operand = lower 16-bit of instruction
PCSrc	PC=PC+4	PC=branch target
MemRead	-	Read data from memory
MemWrite	-	Write data into memory
MemtoReg	Register Write Data from ALU	Register Write Data from data memory

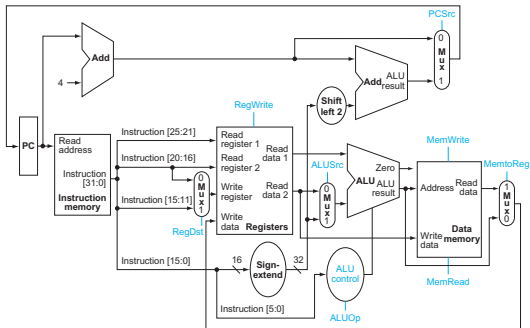

sw rt, 0(rs)

	RegDst	RegWrite	ALUSrc	PCSrc	MemRead	MemWrite	MemtoReg
sw	x	0	1	0	0		


Control Signal	0	1
RegDst	Write register address = rt	Write register address = rd
RegWrite	-	Write register
AluSrc	ALU Second Operand = Read data 2	ALU Second Operand = lower 16-bit of instruction
PCSrc	PC=PC+4	PC=branch target
MemRead	-	Read data from memory
MemWrite	-	Write data into memory
MemtoReg	Register Write Data from ALU	Register Write Data from data memory

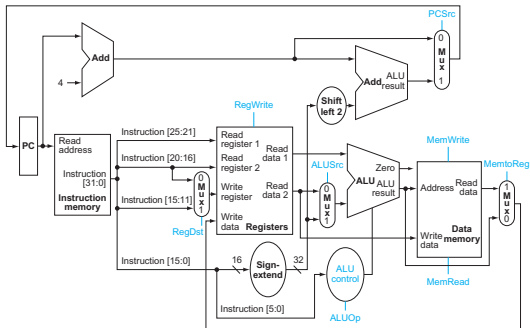

sw rt, 0(rs)

	RegDst	RegWrite	ALUSrc	PCSrc	MemRead	MemWrite	MemtoReg
sw	x	0	1	0	0	1	


Control Signal	0	1
RegDst	Write register address = rt	Write register address = rd
RegWrite	-	Write register
AluSrc	ALU Second Operand = Read data 2	ALU Second Operand = lower 16-bit of instruction
PCSrc	PC=PC+4	PC=branch target
MemRead	-	Read data from memory
MemWrite	-	Write data into memory
MemtoReg	Register Write Data from ALU	Register Write Data from data memory

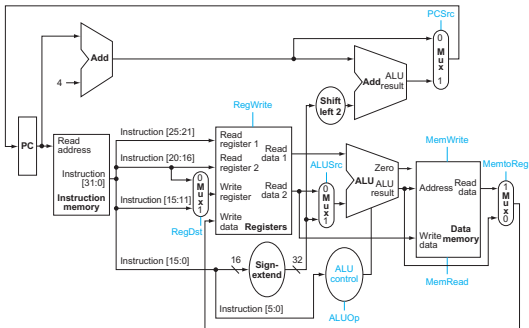

sw rt, 0(rs)

	RegDst	RegWrite	ALUSrc	PCSrc	MemRead	MemWrite	MemtoReg
sw	x	0	1	0	0	1	x


Control Signal	0	1
RegDst	Write register address = rt	Write register address = rd
RegWrite	-	Write register
AluSrc	ALU Second Operand = Read data 2	ALU Second Operand = lower 16-bit of instruction
PCSrc	PC=PC+4	PC=branch target
MemRead	-	Read data from memory
MemWrite	-	Write data into memory
MemtoReg	Register Write Data from ALU	Register Write Data from data memory

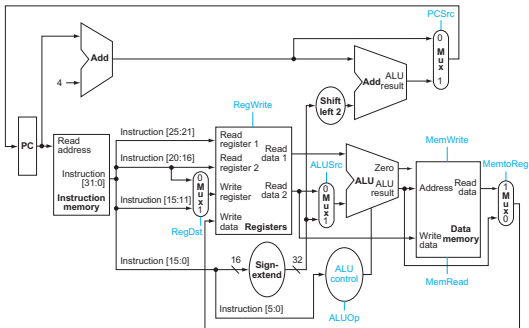

beq rs, rt, address

	RegDst	RegWrite	ALUSrc	PCSrc	MemRead	MemWrite	MemtoReg
beq							


Control Signal	0	1
RegDst	Write register address = rt	Write register address = rd
RegWrite	-	Write register
AluSrc	ALU Second Operand = Read data 2	ALU Second Operand = lower 16-bit of instruction
PCSrc	PC=PC+4	PC=branch target
MemRead	-	Read data from memory
MemWrite	-	Write data into memory
MemtoReg	Register Write Data from ALU	Register Write Data from data memory

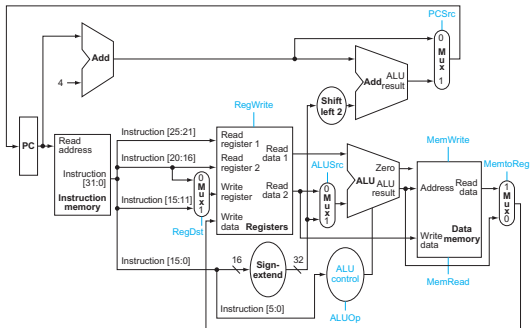

beq rs, rt, address

	RegDst	RegWrite	ALUSrc	PCSrc	MemRead	MemWrite	MemtoReg
beq	x						


Control Signal	0	1
RegDst	Write register address = rt	Write register address = rd
RegWrite	-	Write register
AluSrc	ALU Second Operand = Read data 2	ALU Second Operand = lower 16-bit of instruction
PCSrc	PC=PC+4	PC=branch target
MemRead	-	Read data from memory
MemWrite	-	Write data into memory
MemtoReg	Register Write Data from ALU	Register Write Data from data memory

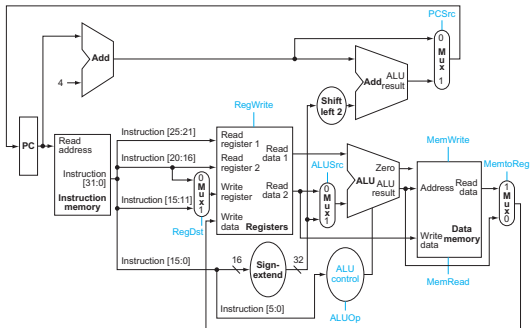

beq rs, rt, address

	RegDst	RegWrite	ALUSrc	PCSrc	MemRead	MemWrite	MemtoReg
beq	x	0					


Control Signal	0	1
RegDst	Write register address = rt	Write register address = rd
RegWrite	-	Write register
AluSrc	ALU Second Operand = Read data 2	ALU Second Operand = lower 16-bit of instruction
PCSrc	PC=PC+4	PC=branch target
MemRead	-	Read data from memory
MemWrite	-	Write data into memory
MemtoReg	Register Write Data from ALU	Register Write Data from data memory

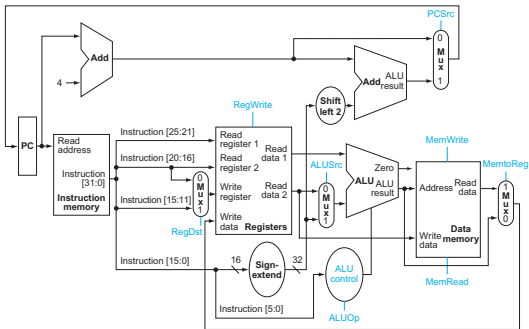

beq rs, rt, address

	RegDst	RegWrite	ALUSrc	PCSrc	MemRead	MemWrite	MemtoReg
beq	x	0	0				


Control Signal	0	1
RegDst	Write register address = rt	Write register address = rd
RegWrite	-	Write register
AluSrc	ALU Second Operand = Read data 2	ALU Second Operand = lower 16-bit of instruction
PCSrc	PC=PC+4	PC=branch target
MemRead	-	Read data from memory
MemWrite	-	Write data into memory
MemtoReg	Register Write Data from ALU	Register Write Data from data memory

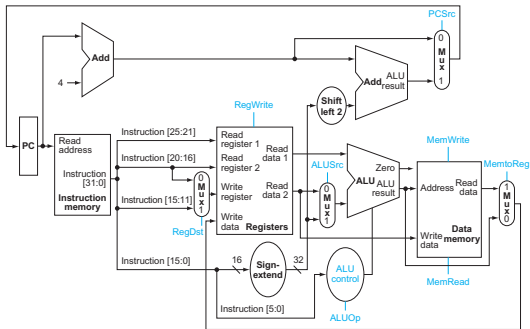

beq rs, rt, address

	RegDst	RegWrite	ALUSrc	PCSrc	MemRead	MemWrite	MemtoReg
beq	x	0	0	1	0		


Control Signal	0	1
RegDst	Write register address = rt	Write register address = rd
RegWrite	-	Write register
AluSrc	ALU Second Operand = Read data 2	ALU Second Operand = lower 16-bit of instruction
PCSrc	PC=PC+4	PC=branch target
MemRead	-	Read data from memory
MemWrite	-	Write data into memory
MemtoReg	Register Write Data from ALU	Register Write Data from data memory

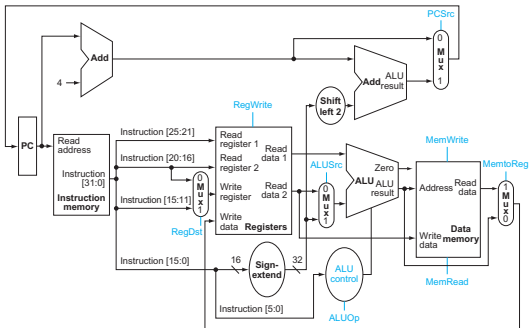

beq rs, rt, address

	RegDst	RegWrite	ALUSrc	PCSrc	MemRead	MemWrite	MemtoReg
beq	x	0	0	1	0	0	


Control Signal	0	1
RegDst	Write register address = rt	Write register address = rd
RegWrite	-	Write register
AluSrc	ALU Second Operand = Read data 2	ALU Second Operand = lower 16-bit of instruction
PCSrc	PC=PC+4	PC=branch target
MemRead	-	Read data from memory
MemWrite	-	Write data into memory
MemtoReg	Register Write Data from ALU	Register Write Data from data memory

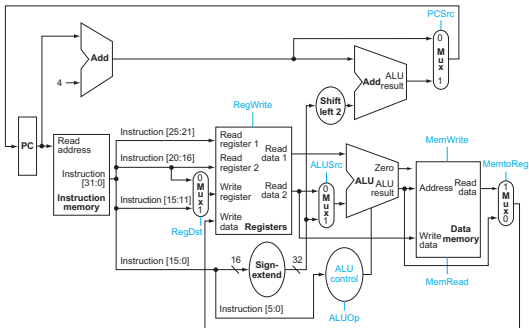


beq rs, rt, address

	RegDst	RegWrite	ALUSrc	PCSrc	MemRead	MemWrite	MemtoReg
beq	x	0	0	1	0	0	x

beq rs, rt, address

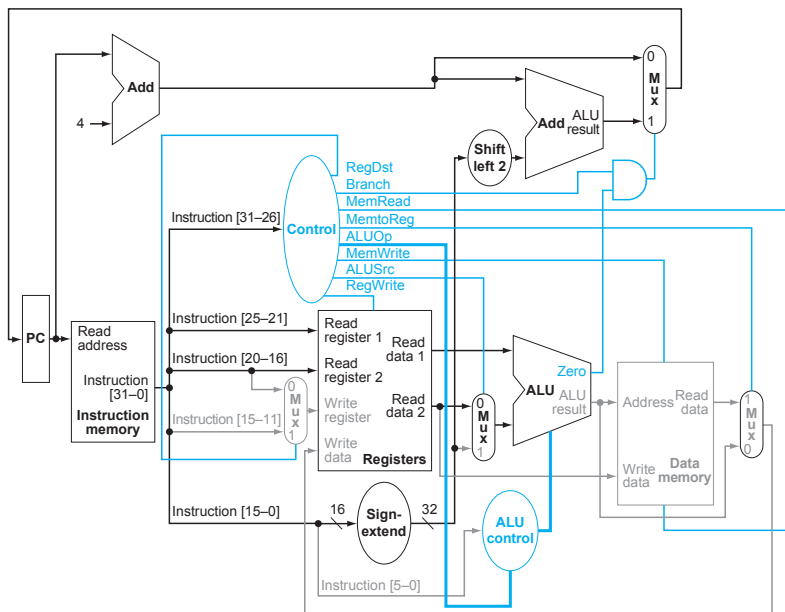


Control Signal	0	1
RegDst	Write register address = rt	Write register address = rd
RegWrite	-	Write register
AluSrc	ALU Second Operand = Read data 2	ALU Second Operand = lower 16-bit of instruction
PCSrc	PC=PC+4	PC=branch target
MemRead	-	Read data from memory
MemWrite	-	Write data into memory
MemtoReg	Register Write Data from ALU	Register Write Data from data memory

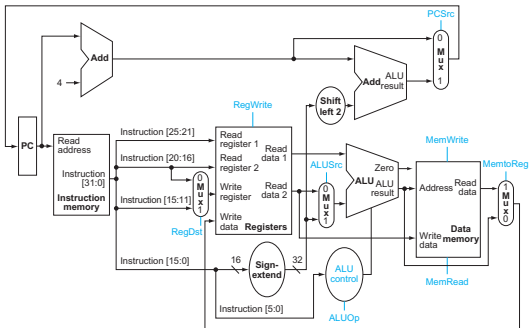

add rd, rs, rt

	RegDst	RegWrite	ALUSrc	PCSrc	MemRead	MemWrite	MemtoReg
add							


Control Signal	0	1
RegDst	Write register address = rt	Write register address = rd
RegWrite	-	Write register
AluSrc	ALU Second Operand = Read data 2	ALU Second Operand = lower 16-bit of instruction
PCSrc	PC=PC+4	PC=branch target
MemRead	-	Read data from memory
MemWrite	-	Write data into memory
MemtoReg	Register Write Data from ALU	Register Write Data from data memory

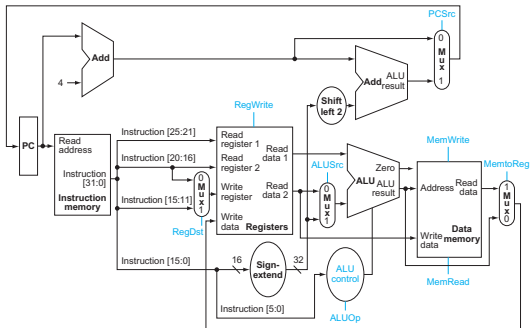

add rd, rs, rt

	RegDst	RegWrite	ALUSrc	PCSrc	MemRead	MemWrite	MemtoReg
add	1						


Control Signal	0	1
RegDst	Write register address = rt	Write register address = rd
RegWrite	-	Write register
AluSrc	ALU Second Operand = Read data 2	ALU Second Operand = lower 16-bit of instruction
PCSrc	PC=PC+4	PC=branch target
MemRead	-	Read data from memory
MemWrite	-	Write data into memory
MemtoReg	Register Write Data from ALU	Register Write Data from data memory

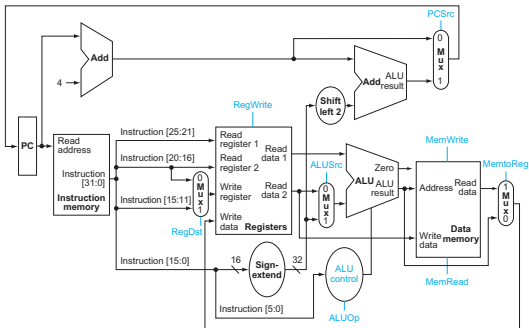

add rd, rs, rt

	RegDst	RegWrite	ALUSrc	PCSrc	MemRead	MemWrite	MemtoReg
add	1	1					


Control Signal	0	1
RegDst	Write register address = rt	Write register address = rd
RegWrite	-	Write register
AluSrc	ALU Second Operand = Read data 2	ALU Second Operand = lower 16-bit of instruction
PCSrc	PC=PC+4	PC=branch target
MemRead	-	Read data from memory
MemWrite	-	Write data into memory
MemtoReg	Register Write Data from ALU	Register Write Data from data memory

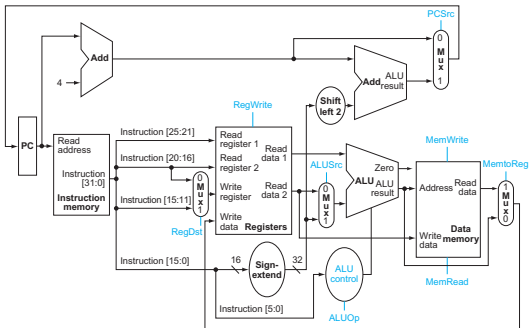

add rd, rs, rt

	RegDst	RegWrite	ALUSrc	PCSrc	MemRead	MemWrite	MemtoReg
add	1	1	0				


Control Signal	0	1
RegDst	Write register address = rt	Write register address = rd
RegWrite	-	Write register
AluSrc	ALU Second Operand = Read data 2	ALU Second Operand = lower 16-bit of instruction
PCSrc	PC=PC+4	PC=branch target
MemRead	-	Read data from memory
MemWrite	-	Write data into memory
MemtoReg	Register Write Data from ALU	Register Write Data from data memory

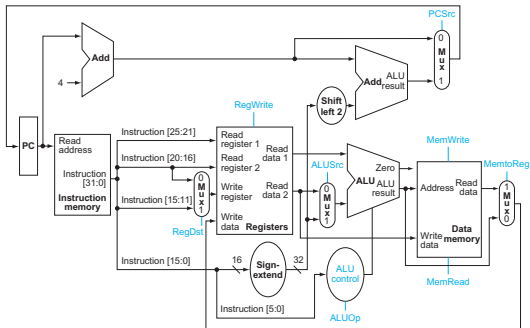

add rd, rs, rt

	RegDst	RegWrite	ALUSrc	PCSrc	MemRead	MemWrite	MemtoReg
add	1	1	0	0	MemRead		


Control Signal	0	1
RegDst	Write register address = rt	Write register address = rd
RegWrite	-	Write register
AluSrc	ALU Second Operand = Read data 2	ALU Second Operand = lower 16-bit of instruction
PCSrc	PC=PC+4	PC=branch target
MemRead	-	Read data from memory
MemWrite	-	Write data into memory
MemtoReg	Register Write Data from ALU	Register Write Data from data memory

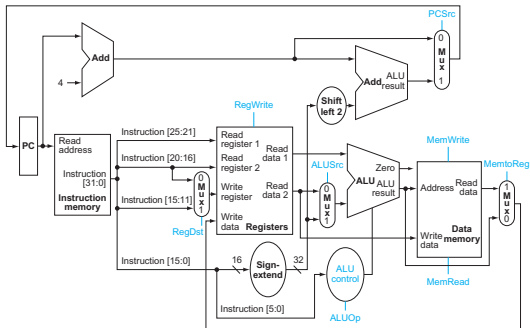

add rd, rs, rt

	RegDst	RegWrite	ALUSrc	PCSrc	MemRead	MemWrite	MemtoReg
add	1	1	0	0	0		


Control Signal	0	1
RegDst	Write register address = rt	Write register address = rd
RegWrite	-	Write register
AluSrc	ALU Second Operand = Read data 2	ALU Second Operand = lower 16-bit of instruction
PCSrc	PC=PC+4	PC=branch target
MemRead	-	Read data from memory
MemWrite	-	Write data into memory
MemtoReg	Register Write Data from ALU	Register Write Data from data memory

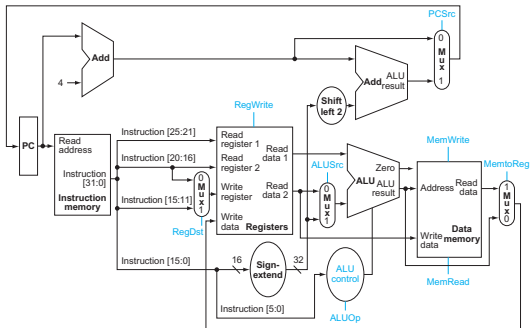

add rd, rs, rt

	RegDst	RegWrite	ALUSrc	PCSrc	MemRead	MemWrite	MemtoReg
add	1	1	0	0	0	0	


Control Signal	0	1
RegDst	Write register address = rt	Write register address = rd
RegWrite	-	Write register
AluSrc	ALU Second Operand = Read data 2	ALU Second Operand = lower 16-bit of instruction
PCSrc	PC=PC+4	PC=branch target
MemRead	-	Read data from memory
MemWrite	-	Write data into memory
MemtoReg	Register Write Data from ALU	Register Write Data from data memory

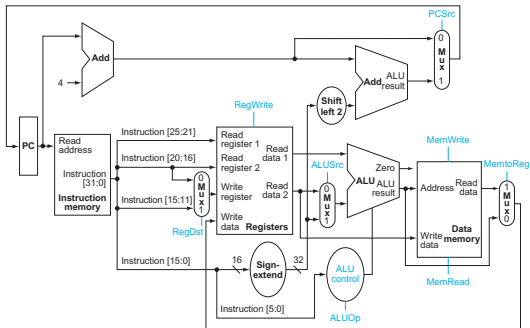

add rd, rs, rt

	RegDst	RegWrite	ALUSrc	PCSrc	MemRead	MemWrite	MemtoReg
add	1	1	0	0	0	0	0


Control Signal	0	1
RegDst	Write register address = rt	Write register address = rd
RegWrite	-	Write register
AluSrc	ALU Second Operand = Read data 2	ALU Second Operand = lower 16-bit of instruction
PCSrc	PC=PC+4	PC=branch target
MemRead	-	Read data from memory
MemWrite	-	Write data into memory
MemtoReg	Register Write Data from ALU	Register Write Data from data memory

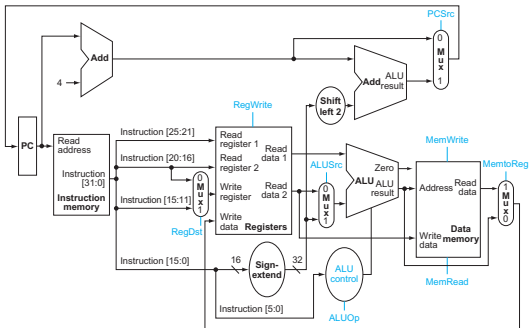

sub rd, rs, rt

	RegDst	RegWrite	ALUSrc	PCSrc	MemRead	MemWrite	MemtoReg
sub							


Control Signal	0	1
RegDst	Write register address = rt	Write register address = rd
RegWrite	-	Write register
AluSrc	ALU Second Operand = Read data 2	ALU Second Operand = lower 16-bit of instruction
PCSrc	PC=PC+4	PC=branch target
MemRead	-	Read data from memory
MemWrite	-	Write data into memory
MemtoReg	Register Write Data from ALU	Register Write Data from data memory

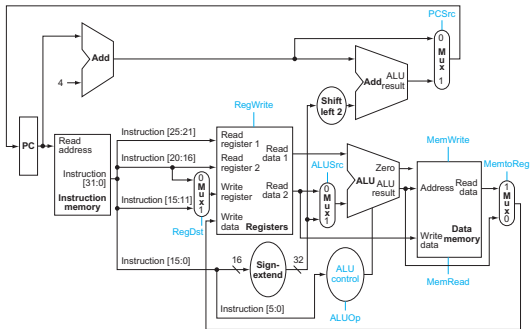

sub rd, rs, rt

sub	RegDst 1	RegWrite	ALUSrc	PCSrc	MemRead	MemWrite	MemtoReg
-----	-------------	----------	--------	-------	---------	----------	----------


Control Signal	0	1
RegDst	Write register address = rt	Write register address = rd
RegWrite	-	Write register
AluSrc	ALU Second Operand = Read data 2	ALU Second Operand = lower 16-bit of instruction
PCSrc	PC=PC+4	PC=branch target
MemRead	-	Read data from memory
MemWrite	-	Write data into memory
MemtoReg	Register Write Data from ALU	Register Write Data from data memory

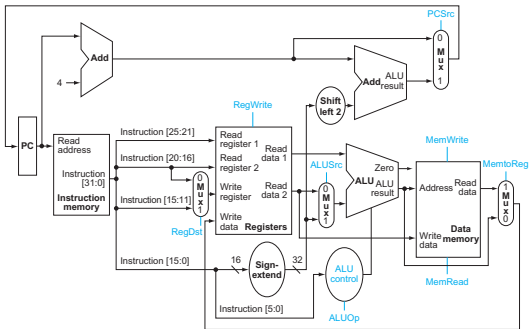

sub rd, rs, rt

	RegDst	RegWrite	ALUSrc	PCSrc	MemRead	MemWrite	MemtoReg
sub	1	1					


Control Signal	0	1
RegDst	Write register address = rt	Write register address = rd
RegWrite	-	Write register
AluSrc	ALU Second Operand = Read data 2	ALU Second Operand = lower 16-bit of instruction
PCSrc	PC=PC+4	PC=branch target
MemRead	-	Read data from memory
MemWrite	-	Write data into memory
MemtoReg	Register Write Data from ALU	Register Write Data from data memory

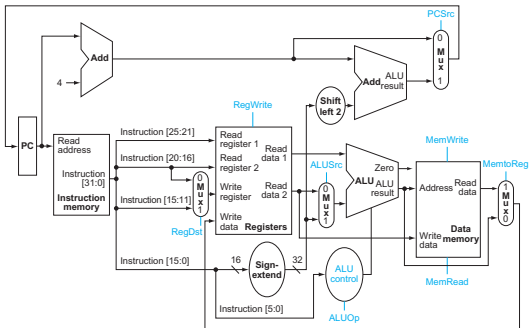

sub rd, rs, rt

	RegDst	RegWrite	ALUSrc	PCSrc	MemRead	MemWrite	MemtoReg
sub	1	1	0				


Control Signal	0	1
RegDst	Write register address = rt	Write register address = rd
RegWrite	-	Write register
AluSrc	ALU Second Operand = Read data 2	ALU Second Operand = lower 16-bit of instruction
PCSrc	PC=PC+4	PC=branch target
MemRead	-	Read data from memory
MemWrite	-	Write data into memory
MemtoReg	Register Write Data from ALU	Register Write Data from data memory

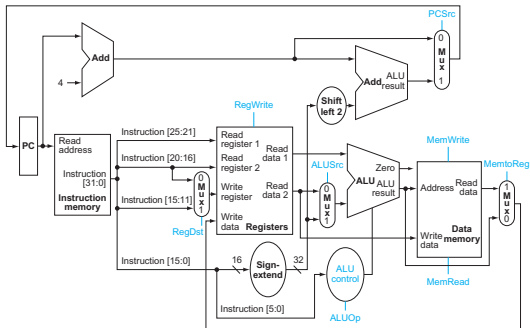

sub rd, rs, rt

	RegDst	RegWrite	ALUSrc	PCSrc	MemRead	MemWrite	MemtoReg
sub	1	1	0	0	0		


Control Signal	0	1
RegDst	Write register address = rt	Write register address = rd
RegWrite	-	Write register
AluSrc	ALU Second Operand = Read data 2	ALU Second Operand = lower 16-bit of instruction
PCSrc	PC=PC+4	PC=branch target
MemRead	-	Read data from memory
MemWrite	-	Write data into memory
MemtoReg	Register Write Data from ALU	Register Write Data from data memory

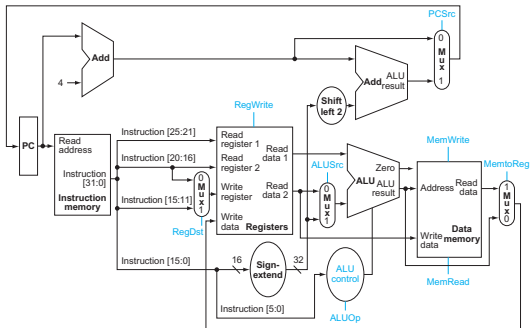

sub rd, rs, rt

	RegDst	RegWrite	ALUSrc	PCSrc	MemRead	MemWrite	MemtoReg
sub	1	1	0	0	0	0	


Control Signal	0	1
RegDst	Write register address = rt	Write register address = rd
RegWrite	-	Write register
AluSrc	ALU Second Operand = Read data 2	ALU Second Operand = lower 16-bit of instruction
PCSrc	PC=PC+4	PC=branch target
MemRead	-	Read data from memory
MemWrite	-	Write data into memory
MemtoReg	Register Write Data from ALU	Register Write Data from data memory

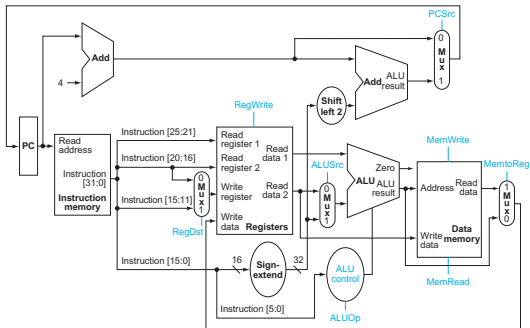

sub rd, rs, rt

	RegDst	RegWrite	ALUSrc	PCSrc	MemRead	MemWrite	MemtoReg
sub	1	1	0	0	0	0	0

Control Signal	0	1
RegDst	Write register address = rt	Write register address = rd
RegWrite	-	Write register
AluSrc	ALU Second Operand = Read data 2	ALU Second Operand = lower 16-bit of instruction
PCSrc	PC=PC+4	PC=branch target
MemRead	-	Read data from memory
MemWrite	-	Write data into memory
MemtoReg	Register Write Data from ALU	Register Write Data from data memory

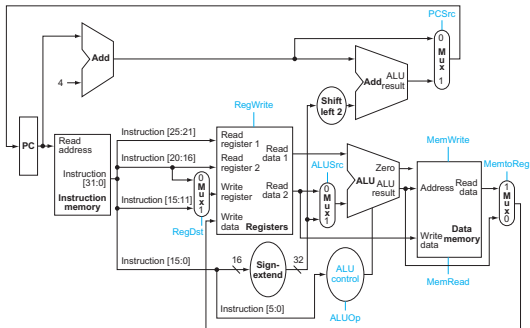


(add/sub/AND/OR/slt) rd, rs, rt

rFormat

RegDst	RegWrite	ALUSrc	PCSrc	MemRead	MemWrite	MemtoReg
1	1	0	0	0	0	0

add rd, rs, rt

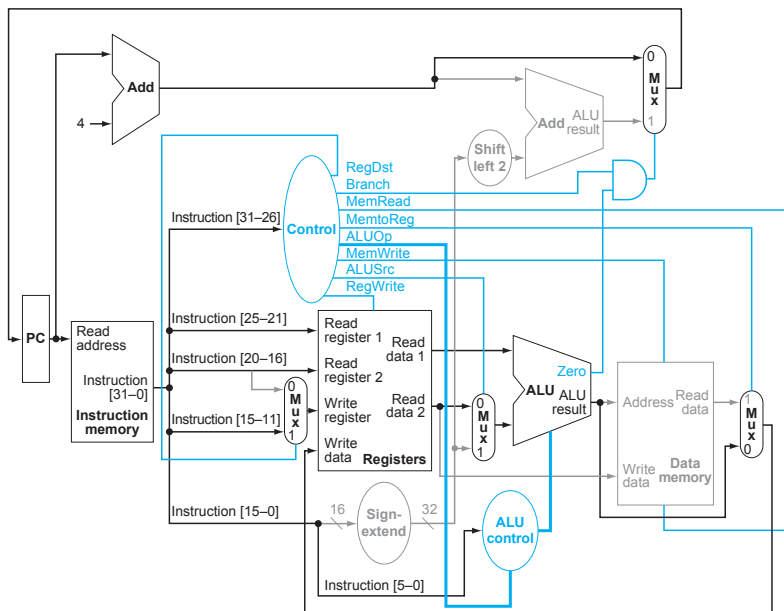

Arithmetic Logic Unit: ALU

ALU Control				Operation
S_3	S_2	S_1	S_0	
0	0	0	0	AND
0	0	0	1	OR
0	0	1	0	ADD
0	1	1	0	SUBTRACT
0	1	1	1	SLT

ALU for different instructions

- ▶ `lw rt, 0(rs)` $\leftrightarrow rt \leftarrow [rs+4 * 0]$,
- ▶ `sw rt, x(rs)` $\leftrightarrow [rs+4 * x] \leftarrow rt$,
- ▶ `beq rs, rt, rd` $\leftrightarrow zero \leftarrow (rs - rt == 0)$
- ▶ `add rs, rt, rd` $\leftrightarrow rd = rs + rt$,
- ▶ `sub rs, rt, rd` $\leftrightarrow rd = rs - rt$,
- ▶ `and rs, rt, rd` $\leftrightarrow rd = rs \& rt$,
- ▶ `or rs, rt, rd` $\leftrightarrow rd = rs | rt$,
- ▶ `slt rs, rt, rd`,

ALU for different instructions

- ▶ `lw rt, 0(rs)` $\leftrightarrow rt \leftarrow [rs+4 * 0]$, add
- ▶ `sw rt, x(rs)` $\leftrightarrow [rs+4 * x] \leftarrow rt$, add
- ▶ `beq rs, rt, rd` $\leftrightarrow zero \leftarrow (rs - rt == 0)$ subtract
- ▶ `add rs, rt, rd` $\leftrightarrow rd = rs + rt$, add
- ▶ `sub rs, rt, rd` $\leftrightarrow rd = rs - rt$, sub
- ▶ `and rs, rt, rd` $\leftrightarrow rd = rs \& rt$, and
- ▶ `or rs, rt, rd` $\leftrightarrow rd = rs | rt$, or
- ▶ `slt rs, rt, rd`, slt

Decoding Instructions

	opcode	function
lw	35	-
sw	43	-
beq	4	-
add	0	32
sub	0	34
AND	0	36
OR	0	37
slt	0	42
j	2	-

Decoding Instructions

Two step Control Unit

	Main Control		function (lsb 6 bit from instruction)						ALU operation	ALU Control			
	ALUOP1	ALUOP0	F ₅	F ₄	F ₃	F ₂	F ₁	F ₀		S ₃	S ₂	S ₁	S ₀
lw	0	0	x	x	x	x	x	x	add	0	0	1	0
sw	0	0	x	x	x	x	x	x	add	0	0	1	0
beq	0	1	x	x	x	x	x	x	sub	0	1	1	0
add	1	x	1	0	0	0	0	0	add	0	0	1	0
sub	1	x	1	0	0	0	1	0	sub	0	1	1	0
AND	1	x	1	0	0	1	0	0	and	0	0	0	0
OR	1	x	1	0	0	1	0	1	or	0	0	0	1
slt	1	x	1	0	1	0	1	0	slt	0	1	1	1

	opcode	function
lw	35	-
sw	43	-
beq	4	-
add	0	32
sub	0	34
AND	0	36
OR	0	37
slt	0	42
j	2	-

ALU Control				Operation
S ₃	S ₂	S ₁	S ₀	
0	0	0	0	AND
0	0	0	1	OR
0	0	1	0	ADD
0	1	1	0	SUBTRACT
0	1	1	1	SLT

Decoding Instructions

Two step Control Unit

	Main Control		function (lsb 6 bit from instruction)						ALU operation	ALU Control			
	ALUOP1	ALUOP0	F ₅	F ₄	F ₃	F ₂	F ₁	F ₀		S ₃	S ₂	S ₁	S ₀
lw	0	0	x	x	x	x	x	x	add	0	0	1	0
sw	0	0	x	x	x	x	x	x	add	0	0	1	0
beq	0	1	x	x	x	x	x	x	sub	0	1	1	0
add	1	x	1	0	0	0	0	0	add	0	0	1	0
sub	1	x	1	0	0	0	1	0	sub	0	1	1	0
AND	1	x	1	0	0	1	0	0	and	0	0	0	0
OR	1	x	1	0	0	1	0	1	or	0	0	0	1
slt	1	x	1	0	1	0	1	0	slt	0	1	1	1

	opcode	function
lw	35	-
sw	43	-
beq	4	-
add	0	32
sub	0	34
AND	0	36
OR	0	37
slt	0	42
j	2	-

ALU Control				Operation
S ₃	S ₂	S ₁	S ₀	
0	0	0	0	AND
0	0	0	1	OR
0	0	1	0	ADD
0	1	1	0	SUBTRACT
0	1	1	1	SLT

Decoding Instructions

Two step Control Unit

	Main Control		function (lsb 6 bit from instruction)						ALU operation	ALU Control			
	ALUOP1	ALUOP0	F ₅	F ₄	F ₃	F ₂	F ₁	F ₀		S ₃	S ₂	S ₁	S ₀
lw	0	0	x	x	x	x	x	x	add	0	0	1	0
sw	0	0	x	x	x	x	x	x	add	0	0	1	0
beq	0	1	x	x	x	x	x	x	sub	0	1	1	0
add	1	x	1	0	0	0	0	0	add	0	0	1	0
sub	1	x	1	0	0	0	1	0	sub	0	1	1	0
AND	1	x	1	0	0	1	0	0	and	0	0	0	0
OR	1	x	1	0	0	1	0	1	or	0	0	0	1
slt	1	x	1	0	1	0	1	0	slt	0	1	1	1

	opcode	function
lw	35	-
sw	43	-
beq	4	-
add	0	32
sub	0	34
AND	0	36
OR	0	37
slt	0	42
j	2	-

ALU Control				Operation
S ₃	S ₂	S ₁	S ₀	
0	0	0	0	AND
0	0	0	1	OR
0	0	1	0	ADD
0	1	1	0	SUBTRACT
0	1	1	1	SLT

Decoding Instructions

Two step Control Unit


	Main Control		function (lsb 6 bit from instruction)						ALU operation	ALU Control			
	ALUOP1	ALUOP0	F ₅	F ₄	F ₃	F ₂	F ₁	F ₀		S ₃	S ₂	S ₁	S ₀
lw	0	0	x	x	x	x	x	x	add	0	0	1	0
sw	0	0	x	x	x	x	x	x	add	0	0	1	0
beq	0	1	x	x	x	x	x	x	sub	0	1	1	0
add	1	x	1	0	0	0	0	0	add	0	0	1	0
sub	1	x	1	0	0	0	1	0	sub	0	1	1	0
AND	1	x	1	0	0	1	0	0	and	0	0	0	0
OR	1	x	1	0	0	1	0	1	or	0	0	0	1
slt	1	x	1	0	1	0	1	0	slt	0	1	1	1

$$S_3 = 0, S_2 = \text{ALUOP1}'\text{ALUOP0} + \text{ALUOP1}F_1, S_2 = \dots$$

	opcode	function
lw	35	-
sw	43	-
beq	4	-
add	0	32
sub	0	34
AND	0	36
OR	0	37
slt	0	42
j	2	-

ALU Control				Operation
S ₃	S ₂	S ₁	S ₀	
0	0	0	0	AND
0	0	0	1	OR
0	0	1	0	ADD
0	1	1	0	SUBTRACT
0	1	1	1	SLT

j address

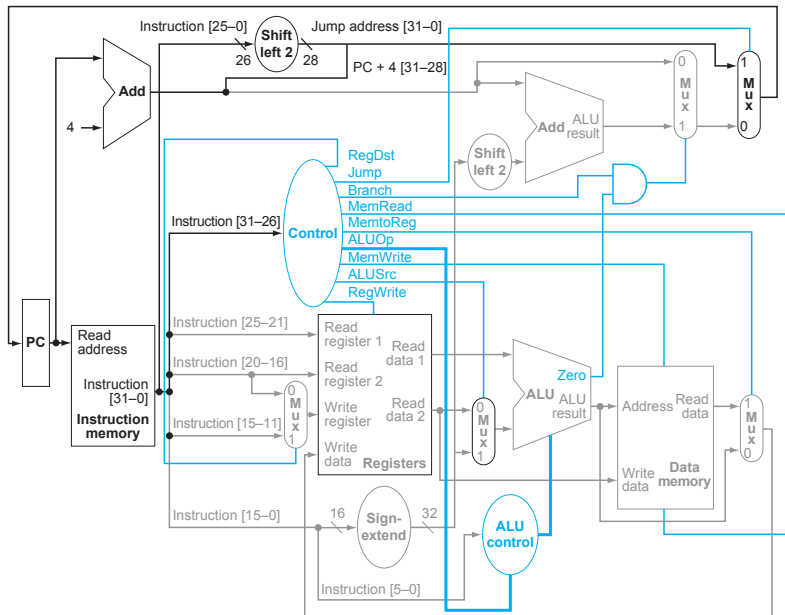

j address

	RegDst	RegWrite	ALUSrc	PCSrc	MemRead	MemWrite	MemtoReg	ALUOP1	ALUOP0	Jump
j	x	x	x	x	x	x	x	x	x	1

Total Main Control Unit

		RegDst	RegWrite	ALUSrc	PCSrc	MemRead	MemWrite	MemtoReg	ALUOP1	ALUOP0	Jump
R-type	0	1	1	0	0	0	0	0	1	x	0
j	2	x	x	x	x	x	x	x	x	x	1
beq	4	x	0	0	1	0	0	x	0	1	0
lw	35	0	1	1	0	1	0	1	0	0	0
sw	43	x	0	1	0	0	1	x	0	0	0

Total Main Control Unit

		RegDst	RegWrite	ALUSrc	PCSrc	MemRead	MemWrite	MemtoReg	ALUOP1	ALUOP0	Jump
R-type	0	1	1	0	0	0	0	0	1	x	0
j	2	x	x	x	x	x	x	x	x	x	1
beq	4	x	0	0	1	0	0	x	0	1	0
lw	35	0	1	1	0	1	0	1	0	0	0
sw	43	x	0	1	0	0	1	x	0	0	0

$2^6 \times 10$ ROM